



Indian Institute of Technology, Bombay
Department of Electrical Engineering

EE 344
Electronic Devices Lab
Milestone 3
Initial subsystem testing review

DSO

Submitted by -

Abhinav Ghunawat
Harsh Lulla
Harsh Choudhary


Guided by -







Prof. Joseph John
Prof. PC Pandey

Contents


1	Design	3
1.1	Circuit Schematic	3
1.2	PCB Layout	5
1.3	CAD Design	6
1.4	GUI	7
1.5	Bill Of Material	8
1.6	Block Diagram	8
2	Abstract and Motivation	8
3	Results and Observations	8
4	Test Results	9
4.1	Voltage Scaling and shifting	9
4.2	I to V converter	10
4.3	Statement of Contribution	10
5	Conclusions and Future Work	11
6	Important Links	11
7	References	11

1.1 Circuit Schematic

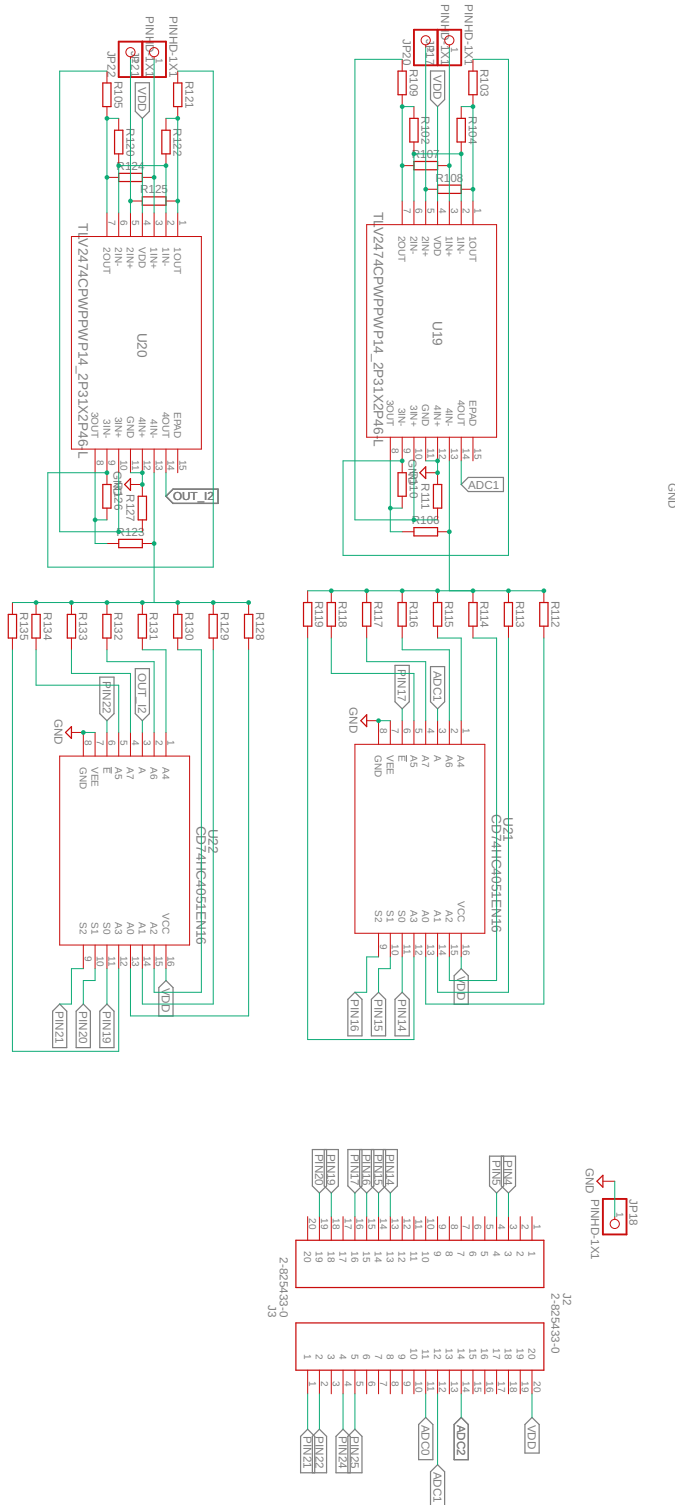

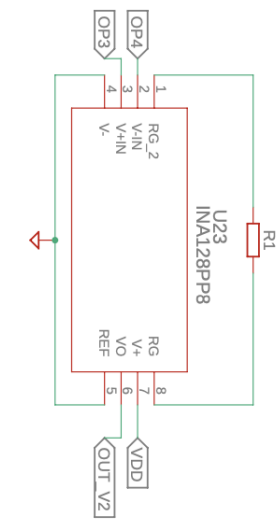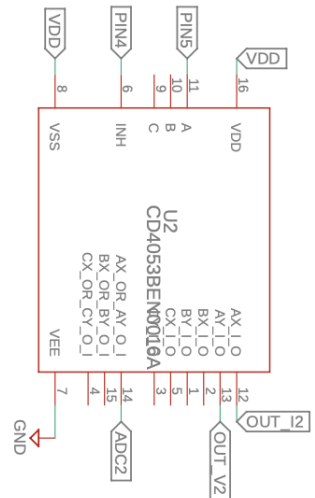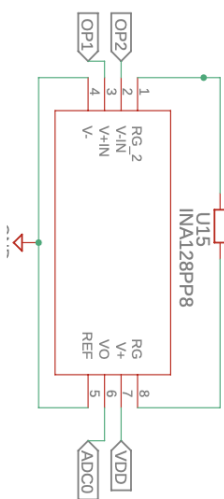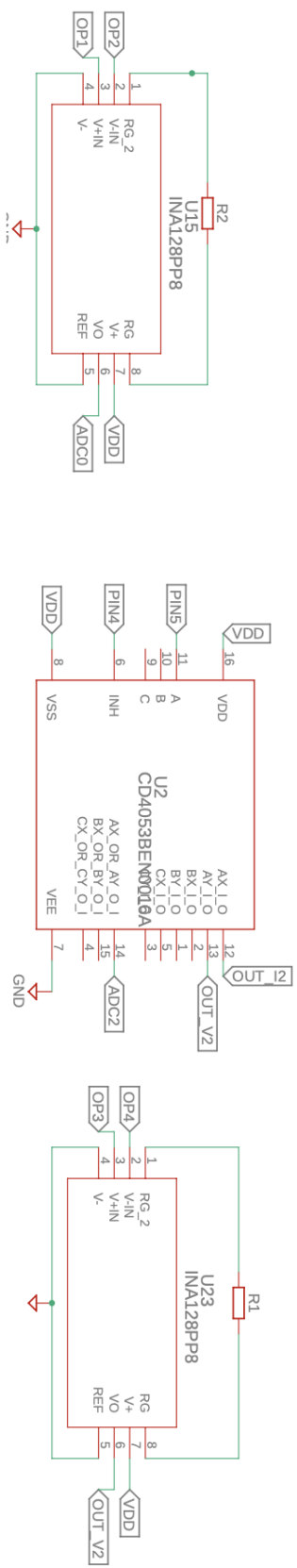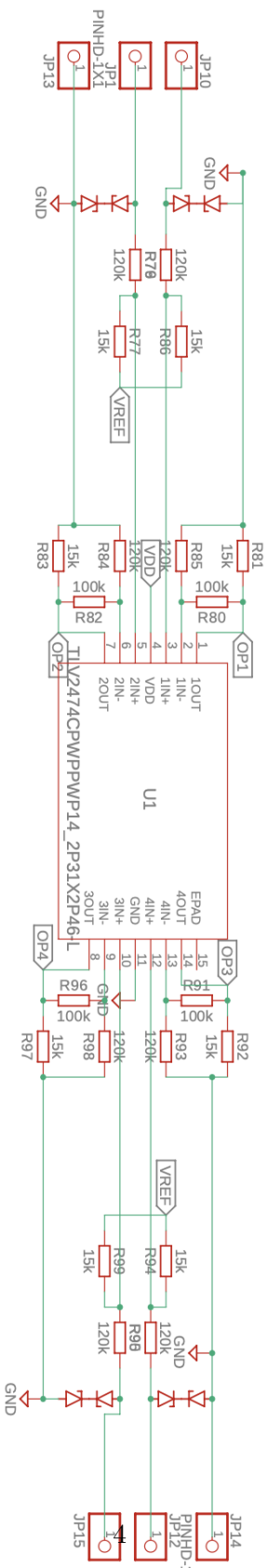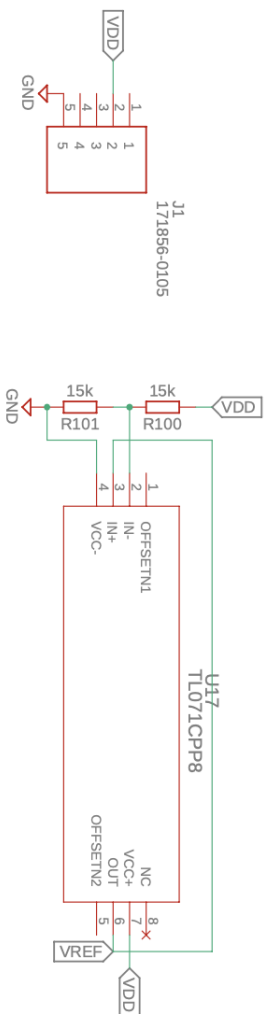

1.2 PCB Layout

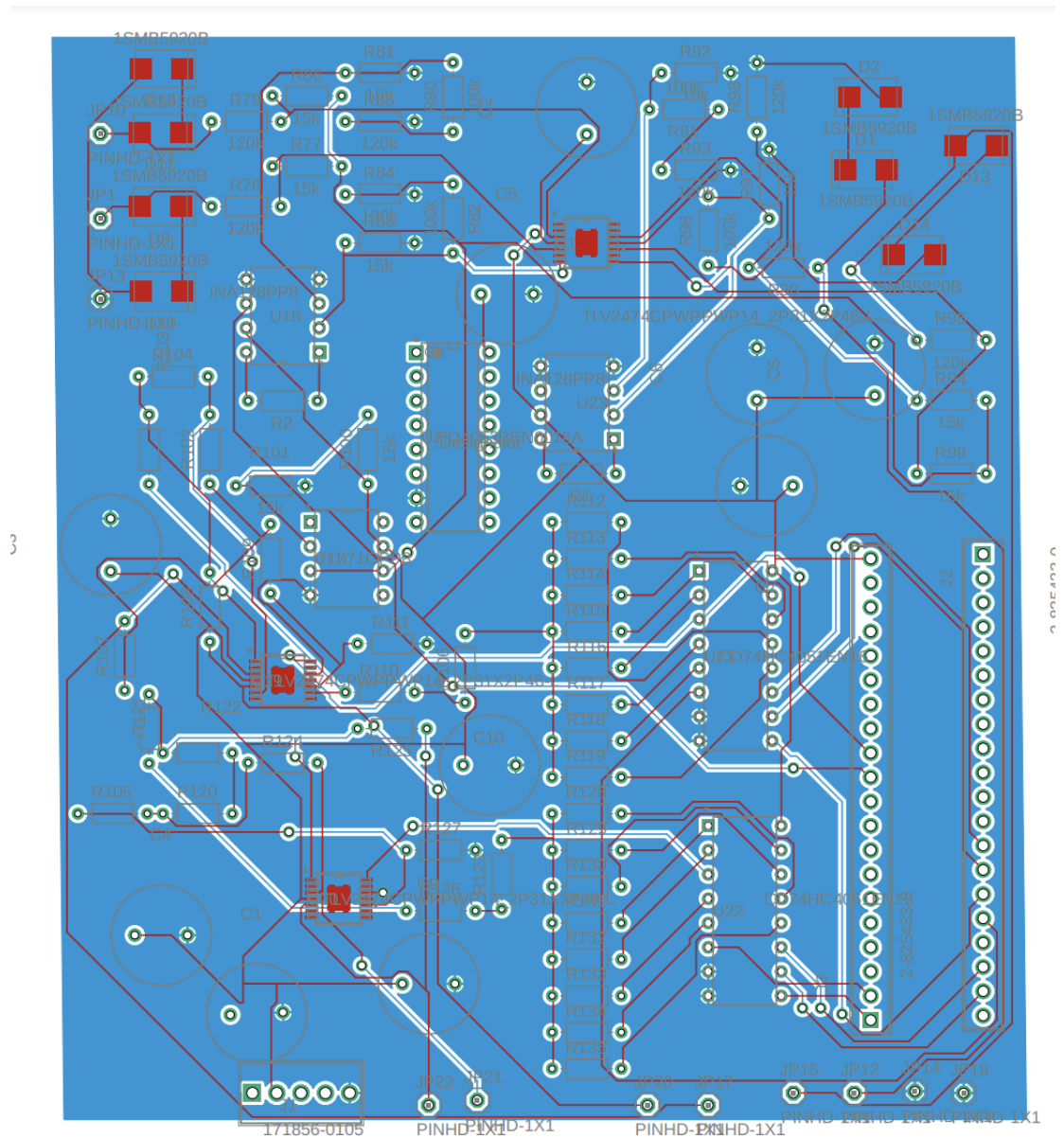

7-03-2023 01:24 f=1.88 C:\Users\harsh\AppData\Local\Temp\Neutron\ElectronFileOutput\7564\hrrd-088ce19c-1a8f-49ee-b9a7-8ef6

Figure 1:

1.3 CAD Design

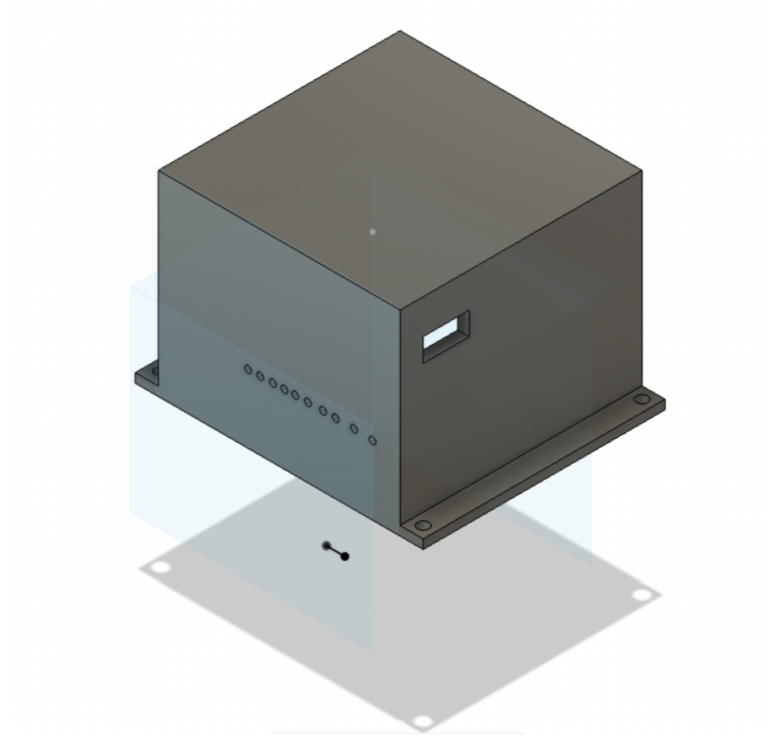


Figure 2: Home View

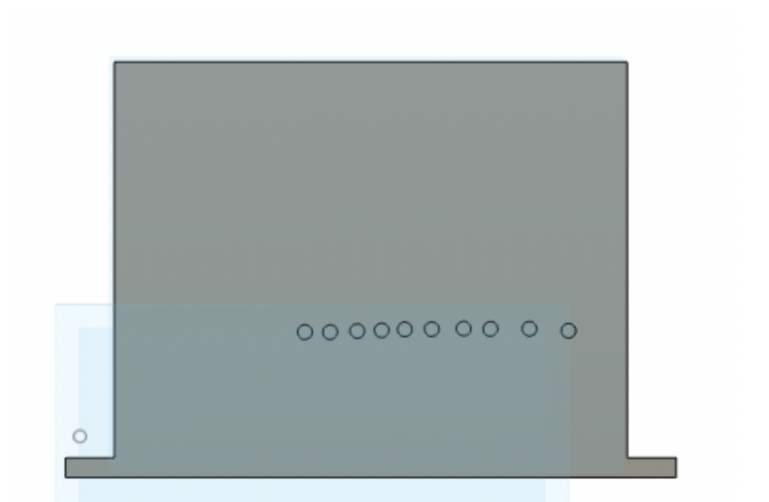


Figure 3: Front View

1.4 GUI

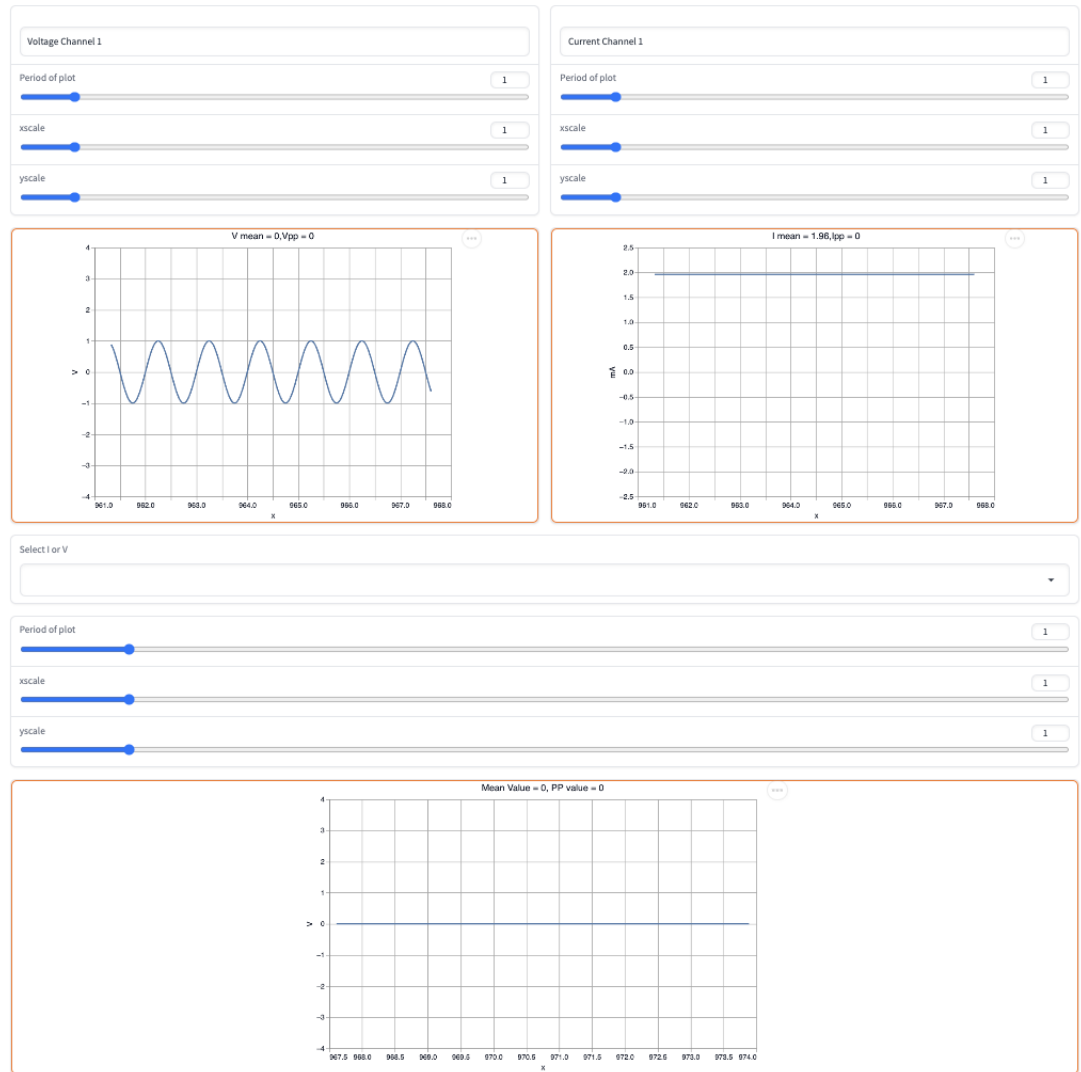


Figure 4: Web Based GUI

1.5 Bill Of Material

ITEMS	Quantity
TLV2474CPWP	2
INA128P	2
TL071CP	4
RPI PICO	1
HC05	1
USB Power Supply	1
CD74HC4051E	1

Figure 5: Bill Of Material extracted from Fusion360

1.6 Block Diagram

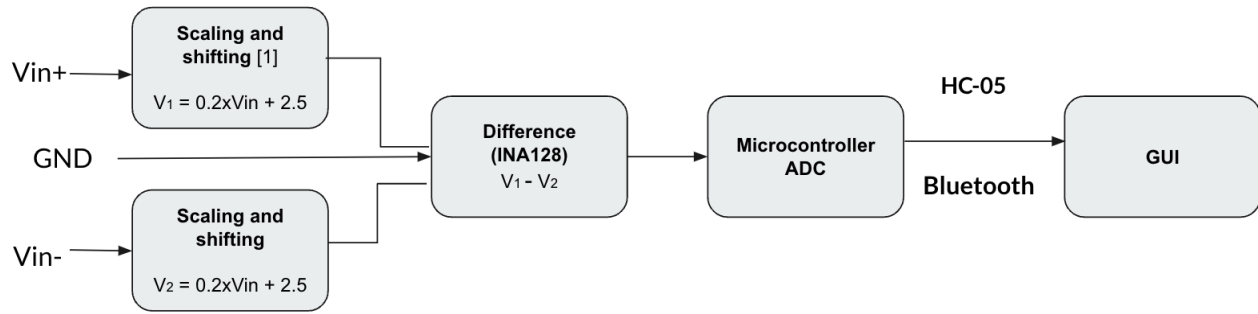


Figure 6: Block Diagram for Differential Voltage Input

2 Abstract and Motivation

Generally, Oscilloscope are bulky and can measure only single-sided voltage, We planned to make portable, Bluetooth-based oscilloscopes for differential inputs

Oscilloscope can not measure current, thus in this project, we planned to measure differential current and voltage using the device

It gives good exposure to different aspects of different fields including Analog front-end Designing, microcontroller programming, GUI designing, Bluetooth Communication, PCB designing and 3-D packaging

3 Results and Observations

We targetted to achieve the following Results

- Differential Input Voltage Range: -4V to 4V
- Differential Currential Sensing: 2.5mA

- Accuracy of more than 0.2V, 0.15mA
- 5V USB power supply
- Web Based GUI
- 2 Differential Current Inputs
- 2 Differential Voltage Inputs

We were able to achieve 5 out of them

- Differential Input Voltage Range: -4V to 4V
- Accuracy of more than 0.2V
- 5V USB Power Supply
- Web-Based GUI
- 2 Differential Voltage Inputs

4 Test Results

4.1 Voltage Scaling and shifting

With this circuit, We have scaled it down by a factor of 1/8 and shifted it by 2.5 volts to bring it in the range of 0 to 5. For this purpose we set resistor values as R2, RF equals 15k ohms, and R1, Rg equals 120k ohms

Input Voltage	Expected Output Voltage	Output Voltage
-16	0.5	0.56
-8	1.5	1.49
-4	2	1.93
4	3	2.95
8	3.5	3.47
12	4	4.02
16	4.5	4.34
20	5	4.95

4.2 I to V converter

We are getting unpredictable outputs for this, till now, we have tried it on simulation tool and on breadboard.

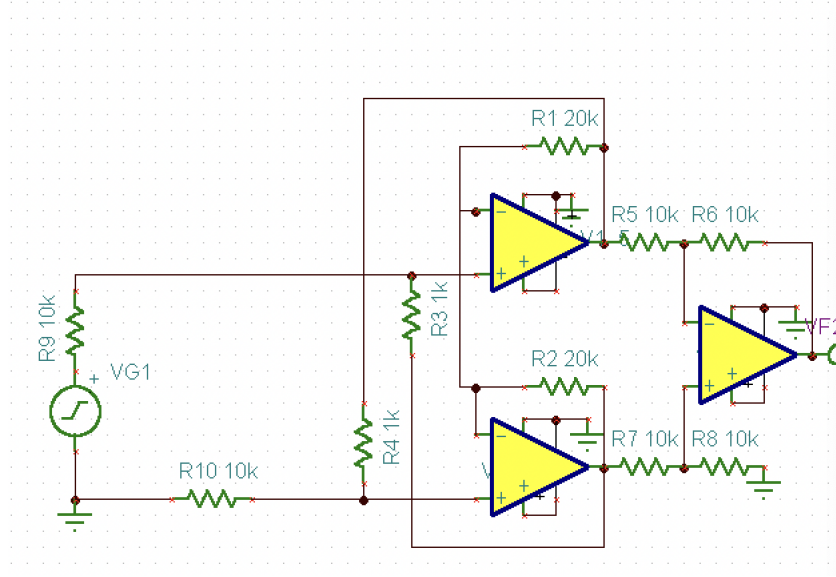


Figure 7: I to V conversion Circuit for simulation in Tina-Ti

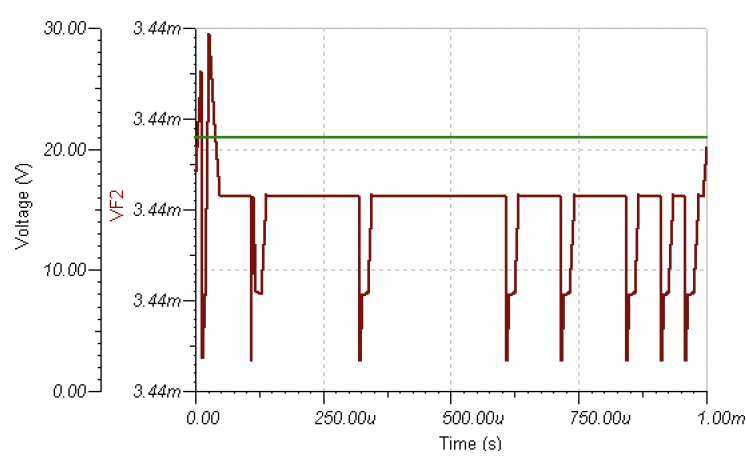


Figure 8: Simulation Results

4.3 Statement of Contribution

- Harsh Choudhary: Designing, Testing, Soldering, Report Making, Schematic Making, Pcb Desgning, Programming Microcontroller, Making GUI
- Abhinav Ghunawat: 3D packaging, Current-Voltage Convertor Testing
- Harsh Lulla: PCB designing, Schematic, Testing

5 Conclusions and Future Work

- More than 3 weeks were spent in searching for the I to V converter and it was tested multiple times by all 3 groups but it did not work.
- For using bluetooth module, MacOS is the best option, windows and ubuntu have multiple complications
- We can increase the input voltage range by increasing the voltage of the power supply and using rail-to-rail opamp
- We can increase the accuracy by reducing the scale-down factor and by using digital-pots for scaling

6 Important Links

- Github Repository
<https://github.com/HC1608/Differential-Input-Oscilloscope>
- Demo-Video
<https://shorturl.at/ltX04>
- Presentation
<https://rb.gy/5xjz2>

7 References

1. Guide for Rpi pico <https://projects.raspberrypi.org/en/projects/getting-started-with-the-pico/3>
2. Guide for Bluetooth <https://howtomechatronics.com/tutorials/arduino/arduino-and-hc-05-bluetooth-module-tutorial/>
3. Guide for Debugging Bluetooth <https://www.verizon.com/support/knowledge-base-20605/>
4. Documentation for the GUI <https://gradio.app/docs/>
5. I to V converter from Pg no.156 Burr-Brown-The handbook of linear IC applications
6. I to V conversion using sense resistance, application note of INA 240
7. Voltage Converter and shifter from Section 4-9 Op Amps for Everyone by Ron Mancini